



Dual H-Bridge - L298 Breakout Board - Homemade

Hey kenlyau, you still need to verify your account.

by BIGDOG1971 (/member/BIGDOG1971/) in arduino (/technology/arduino/)

Write an Instructable (/about/create.jsp)

You ▾ (/you/)

Classes (/classes/)

Download

Contests (/contest/)

Forums (/community/category/Group=all&category=all)

6 Steps

Answers (/tag/type=question?sort=RECENT)

Teachers (/teachers/)

Holiday Gifts (/gifts/)

+ Collection

I Made it!

Favorite

Share ▾

Flag

Dual H-Bridge

L298N Breakout Board

By Marcelo Moraes
BIGDOG1971

(https://cdn.instructables.com/ES6K7TEU/D9BI/NMI/ES6K7TEU/D9BI/NMI/MEDIUM.jpg)

This is my homemade Dual H-Bridge using the IC L298N.

For control DC motors or step Motors ao other purposes just like you need.

Others projects:

<https://www.instructables.com/id/LINUSBot-Line-Follower-Robot/>
<https://www.instructables.com/id/Basic-Principles/>
<https://www.instructables.com/id/PINGBot-Explorer-Robot/>
<https://www.instructables.com/id/3x3x3-LED-Cube-1/>
<https://www.instructables.com/id/LINUSBot-Line-Follower-Robot-with-PID-control/>



Breakout L298N.ppt

Download (https://cdn.instructables.com/ORIG/FGP/QA4T/HD4VDEJR/FGPQA4THD4VDEJR.ppt)

(https://cdn.instructables.com/ORIG/FGP/QA4T/HD4VDEJR/FGPQA4THD4VDEJR.ppt)

Step 1: Hardware and Materials


About This Instructable

94,832 views

105 favorites

Posted:
Feb 13, 2013

License:

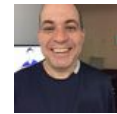

BIGDOG1971
(/member/BIGDOG1971/)
Arduino By Myself
(http://arduinobymyself.blogspot


(/member/BIGDOG1971/) 294

Bio: I am 43 years old and I live in Brazil. I am a Telecommunication / Electronics Engineer. Sixteen years acting in the industry of "Telecommunication and ...
More » (/member/BIGDOG1971/)


More by BIGDOG1971:



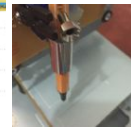(/id/Arduino-Propeller-Message-Display-POV/)



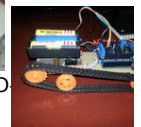(/id/ARDUINO by-Myself-Mini-CNC-Plotter/)



(/id/Arduino-ROVERBot/)

Add instructable to:

Group

Dual H Bridge L298 Breakout Board - Homemade

BIGDOG1971 (/member/BIGDOG1971/) in arduino (/technology/arduino/)

1 x perf board 13x26 holes (3,5 x 7,0 cm)

Download 3D Model (Dual-H-Bridge-L298-Breakout-Board-Homemade/)

1 x 8 Header female connector for Arduino



1 x L298N (Multiwatt15)

8 x 1N4001 Diode

2 x 100nF capacitor

2 x 0,470hm x 1W Resistor

Wire (green and blue colors)

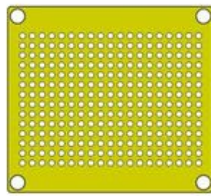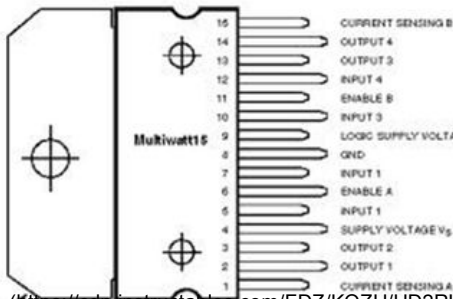

6 Steps


+ Collection

I Made it!

Favorite

Share

Flag

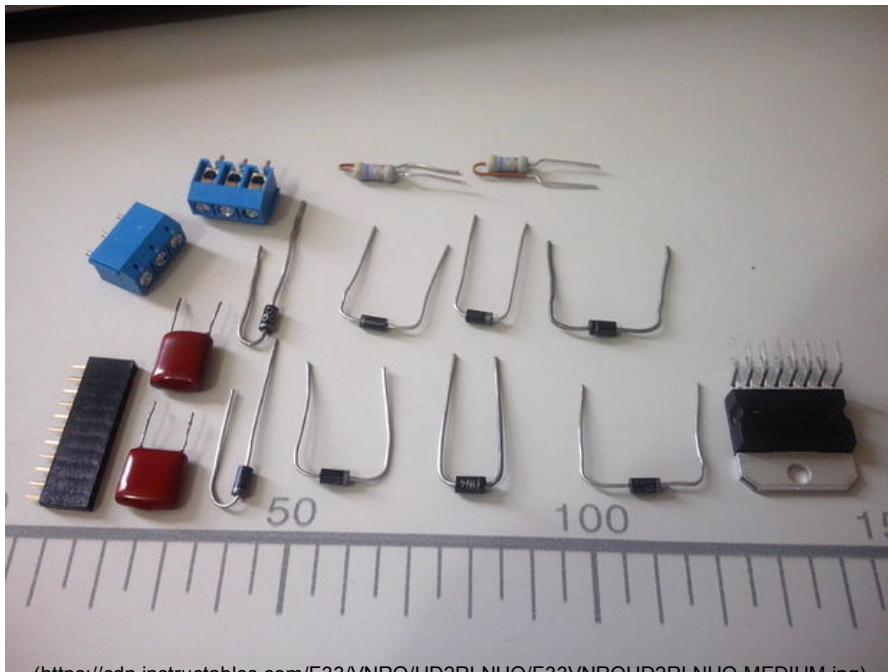

COMPONENTS:

1 x perf board 13x26 holes (3,5 x 7,0 cm)

2 x AK300/3 connector

1 x 8 Header female connector for Arduino

1 x L298N (Multiwatt15)

8 x 1N4001 Diode

2 x 100nF capacitor


2 x 0,470hm x 1W Resistor

Wire (green and blue colors)

Step 2: Schematic

Dual H-Bridge - L298 Breakout Board - Homemade

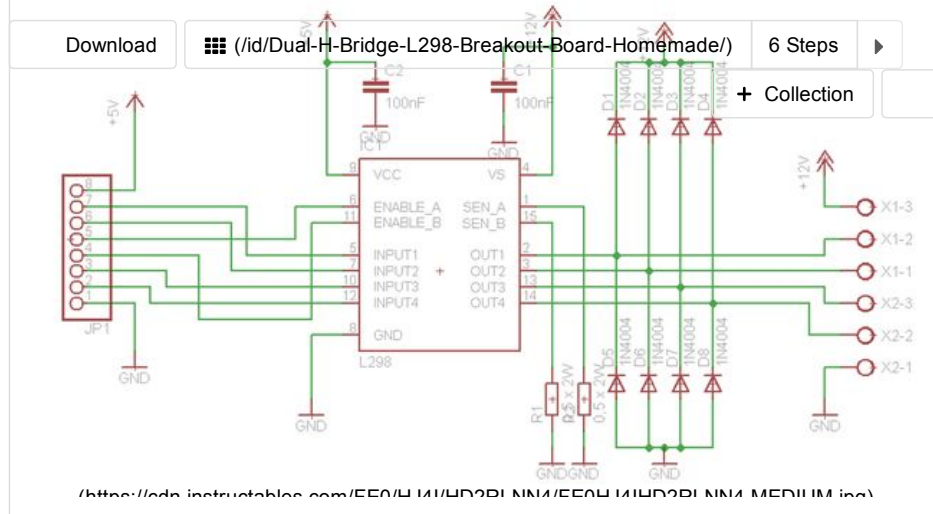by BIGDOG1971 (member/BIGDOG1971/) in arduino (/technology/arduino/)




This is the basic schematic. It works perfectly.

A more advanced schematic and board for eagle cad, you can download from the link below.

http://www.4shared.com/file/T17oVW-z/PONTE_H_L298N.html
(http://www.4shared.com/file/T17oVW-z/PONTE_H_L298N.html)

http://www.4shared.com/file/6VdOTgv5/PONTE_H_L298N.html
(http://www.4shared.com/file/6VdOTgv5/PONTE_H_L298N.html)

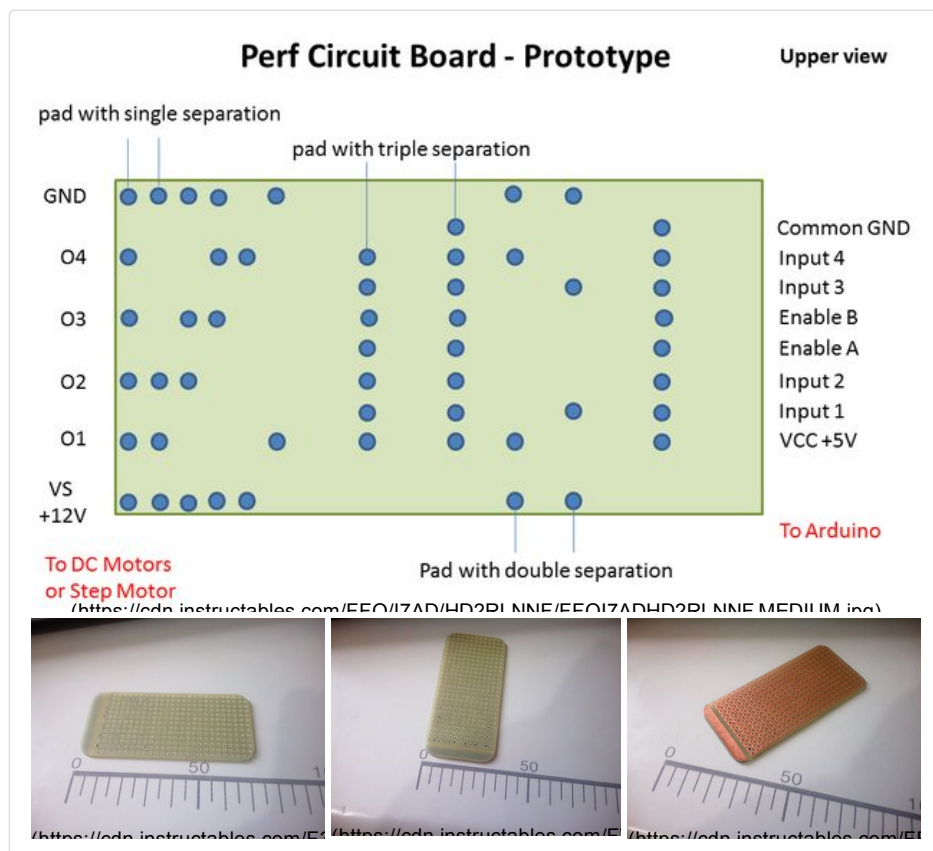Step 3: 1st Step - Perfboard, Holes Location



Download

 (/id/Dual-H-Bridge-L298-Breakout-Board-Homemade/)

6 Steps

▶

+ Collection

I Made it!

♥ Favorite


🔊 Share ▾

🚩

Step 4: 2nd Step - Components


Components layout

Upper view

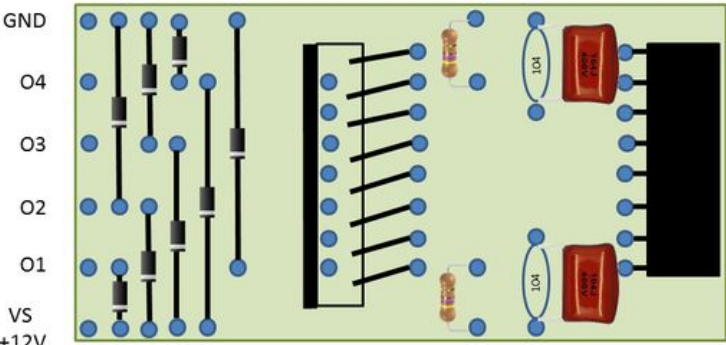


To DC Motors
or Step Motor

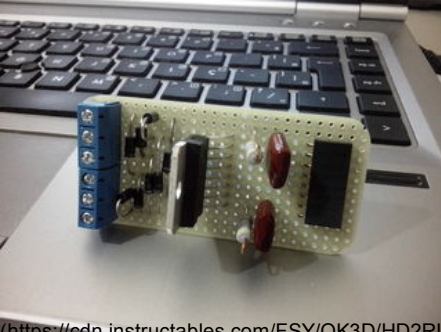
(<https://ada-instructables.com/EQ8/0V1S/HD2PI/N1U/EQ80V1S/HD2PI/N1U/MENIIM/ins>)



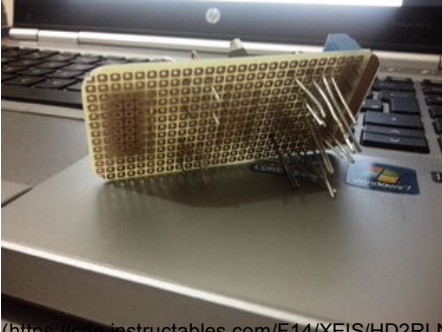
(<https://ada-instructables.com/ESV/OK3D/HD2PI>)



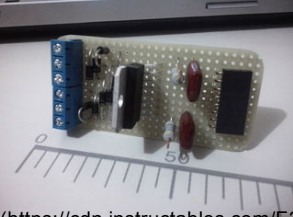
(<https://ada-instructables.com/E44/YEIS/HD2PI>)



(<https://ada-instructables.com/E5>)



(<https://ada-instructables.com/E5>)



(<https://ada-instructables.com/E5>)


Show All 8 Items

After sanding and cleaning the board, put all components in it according of the diagram above and schematic.

For this, bend components properly.

Do the soldering for each group of components independently, for example: diodes first and then connectors and then capacitors and resistors and finally the L298N IC; or in what order you want or you are used to do.


Step 5: 3rd Step - Soldering and Wired Tracks

Download	 (/id/Dual-H-Bridge-L298-Breakout-Board-Homemade/)	6 Steps	
----------	---	---------	---

**Soldered tracks in red color,
on the bottom layer of the circuit board**

<https://leds.instructables.com/E5W/41U0/UD2P1NMA/E5W/41U0UD2P1NMA/MEDIUM.jpg>

Wired Tracks

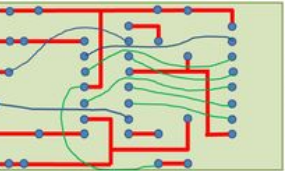


Common GND
Input 4
Input 3
Enable B
Enable A
Input 2
Input 1
VCC +5V


To DC Motors
or Step Motor


Green wire - on the upper layer


Upperview

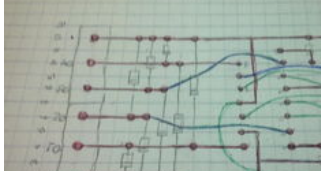
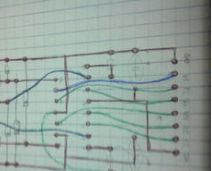
<https://leds.instructables.com/E7C/41ME1/UD2P1NMA/E7C/41ME1UD2P1NMA/MEDIUM.jpg>



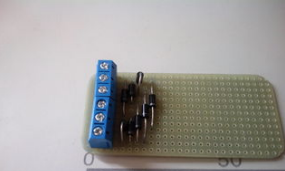



<https://leds.instructables.com/E5W/41U0/UD2P1NMA/E5W/41U0UD2P1NMA/MEDIUM.jpg>

Step 6: 4th Step - Video and Tests

Dual H-Bridge – L298N Breakout Board

BIGDOG1971's Instructable on BIGDOG1971's Arduino (/technic/arduino/)

Hey konyan, you still need to verify your account.



This is my first test of the "Dual H-Bridge" homemade, with the IC-L298N in a Breakout Board.

The cart was controlled by bluetooth (using the "Blue Control" application of the Android market).

Each time we hit in the controls (forward or backward) the DC motor run for 1s, in this way, if we hit twice the motors will run for 2s and so on .
For the left and right, each time we hit the control, the motors will run for 500ms. This temporization can be modified in the program below.

See the entire video for more information; ahh sorry for my English I am studying yet...

<http://youtu.be/0conwkmiAoM> (<http://youtu.be/0conwkmiAoM>)

BlueTooth Controlled cart L298N Breakout Board



/*

#####

#####

File: *BlueTooth_Bot_R1.pde*

Micro controller: *Arduino UNO ou Teensy++ 2.0*

Language: *Wiring / C /Processing /Fritzing / Arduino IDE*